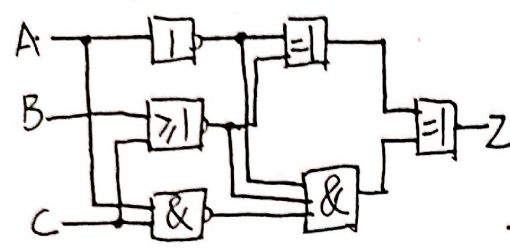


2-2、(a)



解:

$$Z = \bar{A} \oplus \bar{B} + C \oplus \bar{A}C \cdot B\bar{C} \cdot \bar{A}$$


$$Z = \bar{A} \oplus \bar{B} + C \oplus (\bar{A} + \bar{C}) \bar{B} \cdot \bar{C} \cdot \bar{A}$$

$$Z = \bar{A} \oplus \bar{B} + C \oplus \bar{A}\bar{B}\bar{C}$$


真值表:

A	B	C	Z	A	B	C	Z
0	0	0	1	1	0	0	1
0	0	1	1	1	0	1	0
0	1	0	1	1	1	0	0
0	1	1	1	1	1	1	0



2-4.(3) $F_5 = \overline{A\bar{B} + CD}$

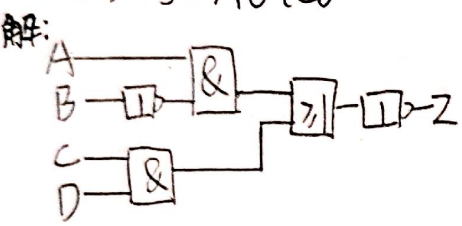

2-5.(1) $F_1 = A\bar{B} + C\bar{D}$

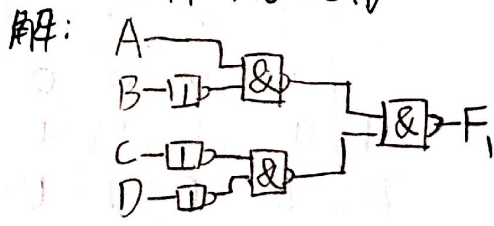

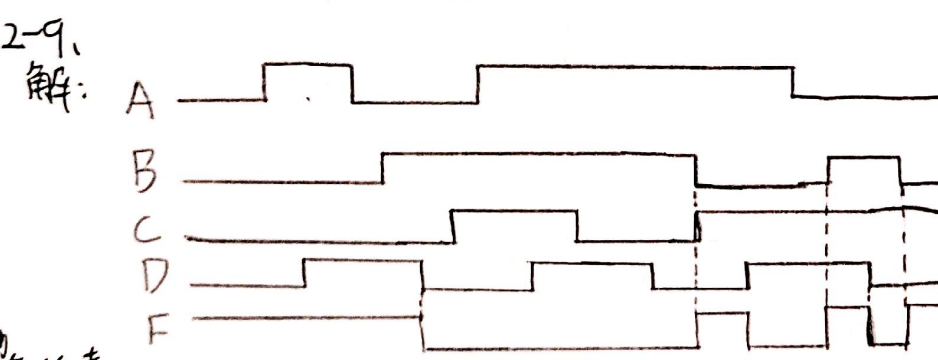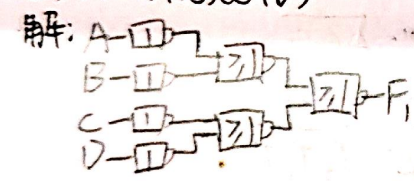2-6.
(1) $F_1 = (A + \bar{B})(\bar{C} + \bar{D})$



真值表:

A	B	C	D	F	A	B	C	D	F
0	0	0	0	1	1	0	0	0	1
0	0	0	1	1	1	0	0	1	1
0	0	1	0	1	1	0	1	0	1
0	0	1	1	0	1	0	1	1	0
0	1	0	0	0	1	1	0	0	0
0	1	0	1	1	1	1	0	1	0
0	1	1	0	0	1	1	1	0	0
0	1	1	1	1	1	1	1	1	0


卡诺图:

AB \ CD	00	01	11	10
00	1	1	0	1
01	0	1	1	0
11	0	0	0	0
10	1	1	0	1

$$F = \bar{B}\bar{C} + \bar{A}BD + \bar{B}\bar{D}$$

$$F = \overline{\bar{B}\bar{C} \cdot \bar{A}\bar{B}D \cdot \bar{B}\bar{D}}$$

电路:

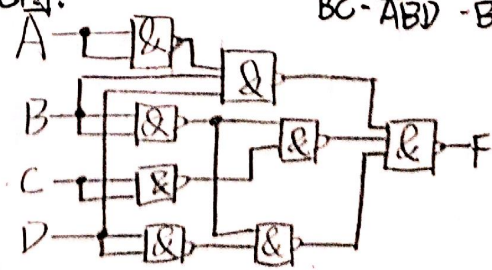

2-13.
解: 真值表: 分别以 A, B, C, D 代表 T_3, T_2, T_1, T_0

A	B	C	D	X	Y	A	B	C	D	X	Y
0	0	0	0	1	0	1	0	0	0	0	0
0	0	0	1	1	0	1	0	0	1	0	0
0	0	1	0	1	0	1	0	1	0	0	0
0	0	1	1	1	0	1	0	1	1	0	1
0	1	0	0	1	0	1	1	0	0	0	1
0	1	0	1	0	0	1	1	0	1	0	1
0	1	1	0	0	0	1	1	1	0	0	1
0	1	1	1	0	0	1	1	1	1	0	1

卡诺图:

X:

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	0	0	0
11	0	0	0	0
10	0	0	0	0

$$X = \overline{A}\overline{B} + \overline{A}\overline{C}\overline{D}$$

$$X = \overline{\overline{A}\overline{B} \cdot \overline{A}\overline{C}\overline{D}}$$

即 $X = \overline{T_3 \cdot T_2} \cdot \overline{T_3 \cdot T_1 \cdot T_0}$

Y

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	0

~~$$Y = \overline{A}\overline{B} + \overline{A}\overline{C}\overline{D}$$~~
$$Y = \overline{A}\overline{B} + \overline{A}\overline{C}\overline{D}$$

~~$$Y = \overline{\overline{A}\overline{B} \cdot \overline{A}\overline{C}\overline{D}}$$~~
$$Y = \overline{A}\overline{B} \cdot \overline{A}\overline{C}\overline{D}$$

~~$$Y = \overline{T_3 \cdot T_2} \cdot \overline{T_3 \cdot T_1 \cdot T_0}$$~~
$$Y = \overline{T_3 \cdot T_2} \cdot \overline{T_3 \cdot T_1 \cdot T_0}$$

电路图:

