

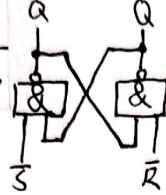
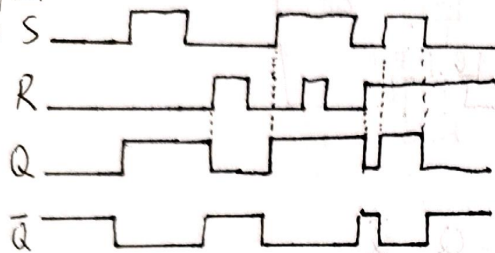


# 便 笺



4-1、  
解:

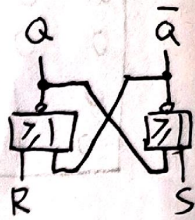



4-2、  
解:

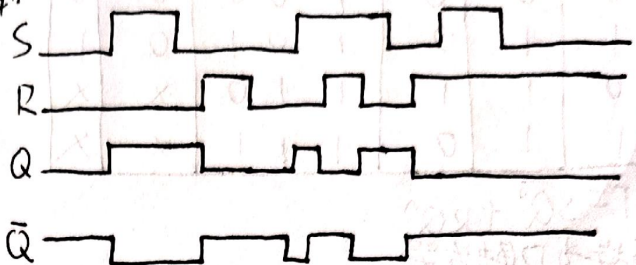


4-3、  
解:

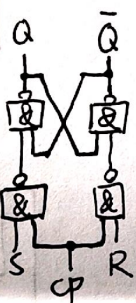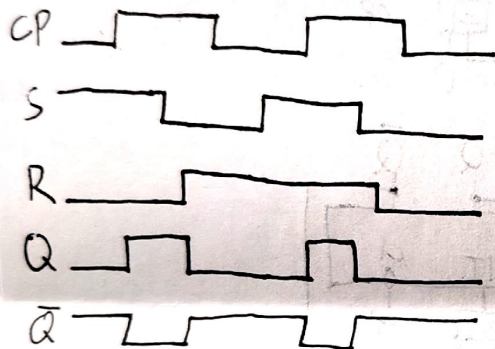


4-4、  
解:

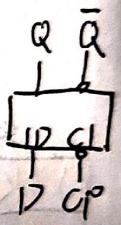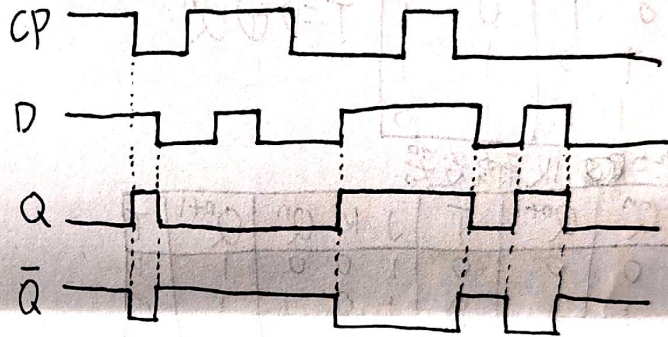

4-8、  
解:

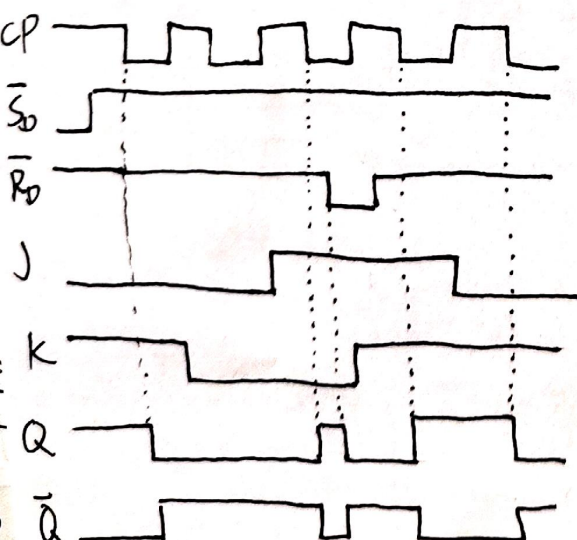

4-9、  
解:

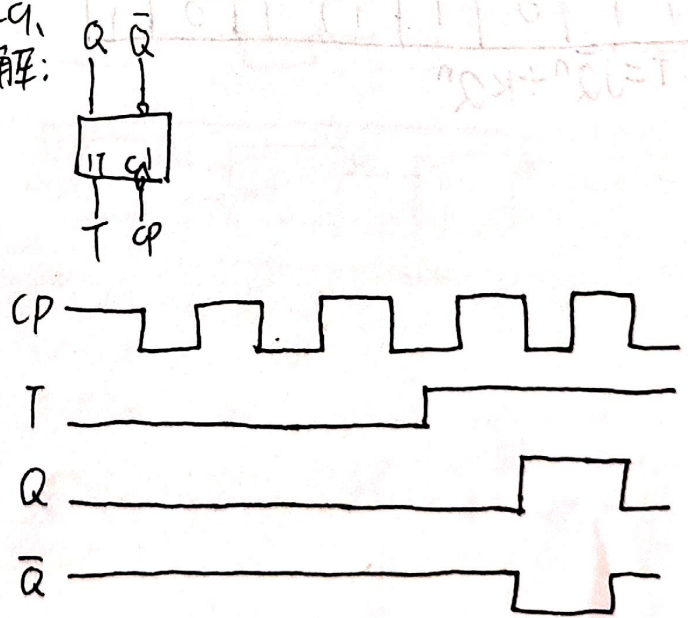

4-1)

解:

$$Q^{n+1} = T\bar{Q}^n + \bar{T}Q^n$$

T触发器转换为RS触发器

R	S	$Q^n$	$Q^{n+1}$	T	R	S	$Q^n$	$Q^{n+1}$	T
0	0	0	0	0	1	0	0	0	0
0	0	1	1	0	1	0	1	0	1
0	1	0	1	1	1	1	0	X	X
0	1	1	1	0	1	1	1	X	X

$$T = S\bar{Q}^n + RQ^n$$

转换为D触发器

D	$Q^n$	$Q^{n+1}$	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0




$$T = D \oplus Q^n$$

转换为JK触发器

J	K	$Q^n$	$Q^{n+1}$	T	J	K	$Q^n$	$Q^{n+1}$	T
0	0	0	0	0	1	0	0	1	1
0	0	1	1	0	1	0	1	1	0
0	1	0	0	0	1	1	0	1	1
0	1	1	0	1	1	1	1	0	1

$$T = J\bar{Q}^n + KQ^n$$

~~4-2)~~

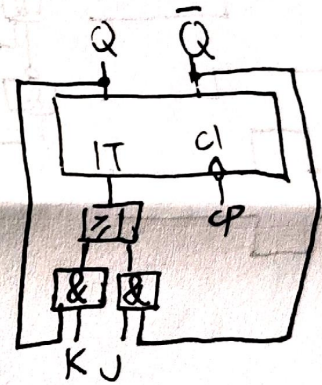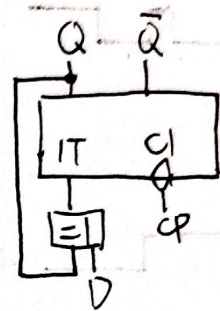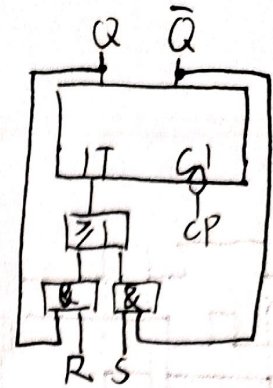

# 便笺

4-12.

解:

(1)  $Q_1^{n+1} = D = \bar{Q}_1^n, CP \downarrow$

(2)

$Q_2^{n+1} = J\bar{Q}_2^n + KQ_2^n = A\bar{Q}_2^n + AQ_2^n = A, CP \downarrow$

(3)

$Q_3^{n+1} = T\bar{Q}_3^n + \bar{T}Q_3^n = T \oplus Q_3^n = A \oplus Q_3^n \oplus Q_3^n = A, CP \downarrow$

(4)


$Q_4^{n+1} = D = A \oplus \bar{Q}_4^n, CP \downarrow$

(5)


$Q_5^{n+1} = J\bar{Q}_5^n + KQ_5^n = (Q_5^n + \bar{Q}_5^n)\bar{Q}_5^n + Q_5^n = \bar{Q}_5^n, CP \downarrow$

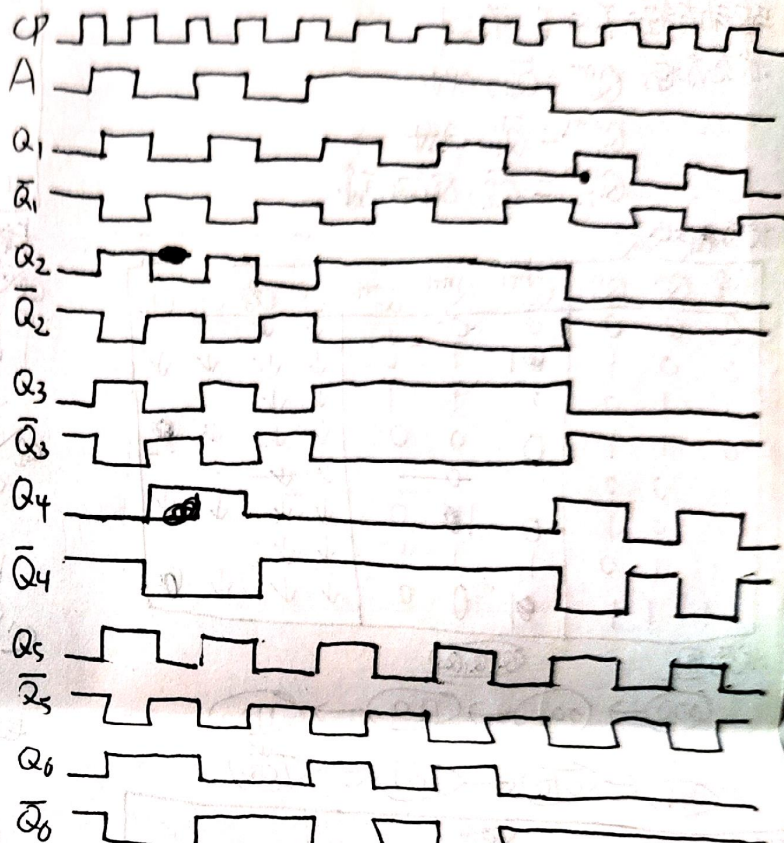(6)

$Q_6^{n+1} = J\bar{Q}_6^n + KQ_6^n = (A + Q_6^n)\bar{Q}_6^n + (\bar{A} + \bar{Q}_6^n)Q_6^n = A\bar{Q}_6^n + \bar{A}Q_6^n = A \oplus Q_6^n, CP \downarrow$



4-13.

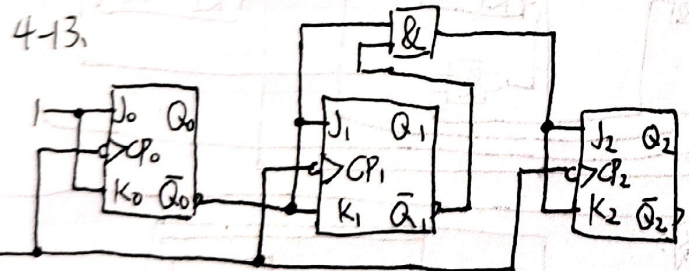

解: 时钟方程:  $CP_0 = CP_1 = CP_2 = CP$


特性方程:  $Q^{n+1} = J\bar{Q}^n + KQ^n$

驱动方程:  $J_0 = 1, J_1 = \bar{Q}_0^n, J_2 = \bar{Q}_0^n \bar{Q}_1^n$


$K_0 = 1, K_1 = \bar{Q}_0^n, K_2 = \bar{Q}_0^n \bar{Q}_1^n$

状态方程:  $Q_0^{n+1} = \bar{Q}_0^n, Q_1^{n+1} = \bar{Q}_0^n \bar{Q}_1^n + Q_0^n Q_1^n, Q_2^{n+1} = \bar{Q}_0^n \bar{Q}_1^n \bar{Q}_2^n + \bar{Q}_0^n \bar{Q}_1^n Q_2^n + Q_0^n Q_1^n \bar{Q}_2^n + Q_0^n Q_1^n Q_2^n$

$Q_2^n$	$Q_1^n$	$Q_0^n$	$Q_2^{n+1}$	$Q_1^{n+1}$	$Q_0^{n+1}$
0	0	0	1	0	1
0	0	1	1	0	0
0	1	0	1	1	1
0	1	1	1	1	0

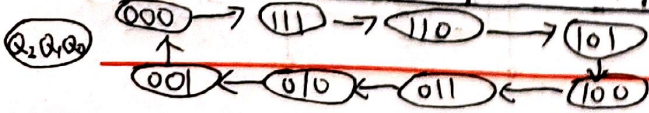

4-14.

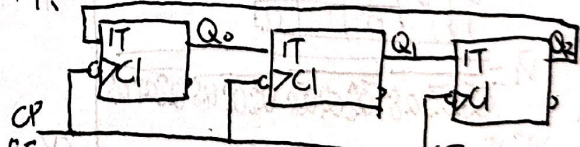


解: 时钟方程:  $CP_0 = CP_1 = CP_2 = CP$

特性方程:  $Q^{n+1} = T\bar{Q}^n + \bar{T}Q^n$

驱动方程:  $T_0 = Q_1^n, T_1 = Q_0^n, T_2 = Q_1^n$


状态方程:  $Q_0^{n+1} = Q_1^n \oplus Q_0^n, Q_1^{n+1} = Q_0^n \oplus Q_1^n, Q_2^{n+1} = Q_1^n \oplus Q_2^n$

$Q_2^n$	$Q_1^n$	$Q_0^n$	$Q_2^{n+1}$	$Q_1^{n+1}$	$Q_0^{n+1}$
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	1	1

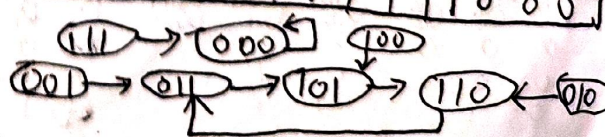

年 月 日

4-15.

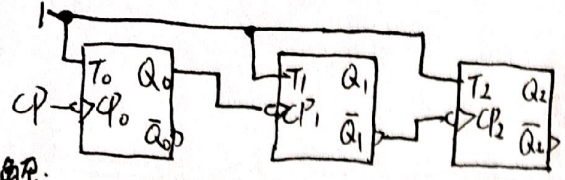

解:

时钟方程:  $CP_0 = CP, CP_1 = Q_0, CP_2 = Q_1$


驱动方程:  $T_0 = T_1 = T_2 = 1$

状态方程:  $Q_0^{n+1} = \bar{Q}_0^n, CP \downarrow$   
 $Q_1^{n+1} = \bar{Q}_1^n, Q_0 \downarrow$   
 $Q_2^{n+1} = \bar{Q}_2^n, Q_1 \downarrow$


状态转换表:

$Q_2^n$	$Q_1^n$	$Q_0^n$	$Q_2^{n+1}$	$Q_1^{n+1}$	$Q_0^{n+1}$	$CP$	$CP_0$	$CP_1$	$CP_2$
0	0	0	1	0	1	↓	↓	↓	↓
0	0	1	1	1	0	↓	↓	↓	↓
0	1	0	0	1	1	↓	↓	↓	↓
0	1	1	0	0	0	↓	↓	↓	↓
1	0	0	1	0	1	↓	↓	↓	↓
1	0	1	0	1	0	↓	↓	↓	↓
1	1	0	1	1	1	↓	↓	↓	↓
1	1	1	0	0	0	↓	↓	↓	↓

状态图

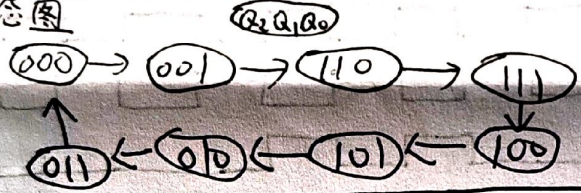


卡诺图:

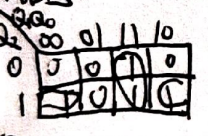

$P_2 = Q_2Q_0 + Q_2Q_1$




$P_1 = Q_1Q_0 + Q_1Q_2$

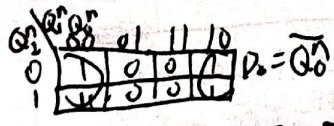

$P_0 = Q_0Q_1$


4-18.

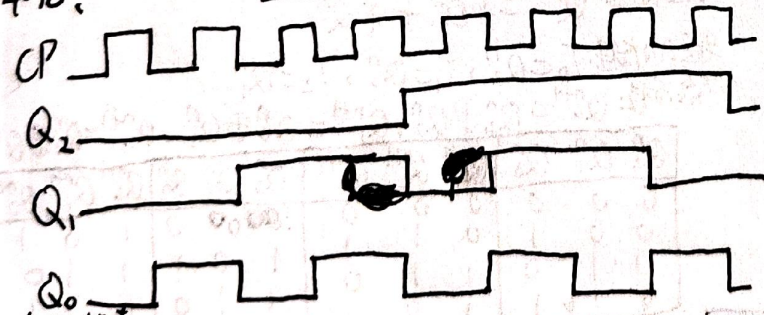

状态转换表:

$Q_2^n$	$Q_1^n$	$Q_0^n$	$Q_2^{n+1}$	$Q_1^{n+1}$	$Q_0^{n+1}$	$D_2$	$D_1$	$D_0$
0	0	0	0	1	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
0	1	1	1	0	1	1	0	1
1	0	0	0	1	1	0	1	0
1	0	1	0	1	0	0	1	1
1	1	0	1	1	0	1	1	0
1	1	1	1	1	1	1	1	1


4-17.

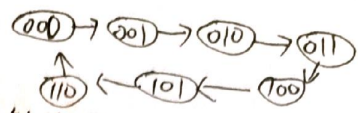


解: 状态转换图:

$Q_2^n$	$Q_1^n$	$Q_0^n$	$Q_2^{n+1}$	$Q_1^{n+1}$	$Q_0^{n+1}$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	X	X	X	X	X	X	X	X	X

卡诺图:

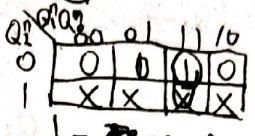


$J_2 = Q_2Q_0 + Q_2Q_1$

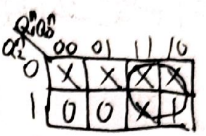


$K_2 = Q_1$




$J_1 = Q_0$

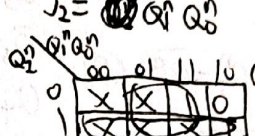

$K_1 = Q_0 + Q_2$

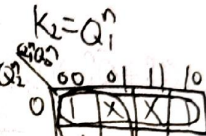


$J_0 = Q_2 + Q_1$

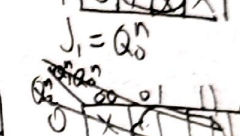

$K_0 = 1$

电路图:

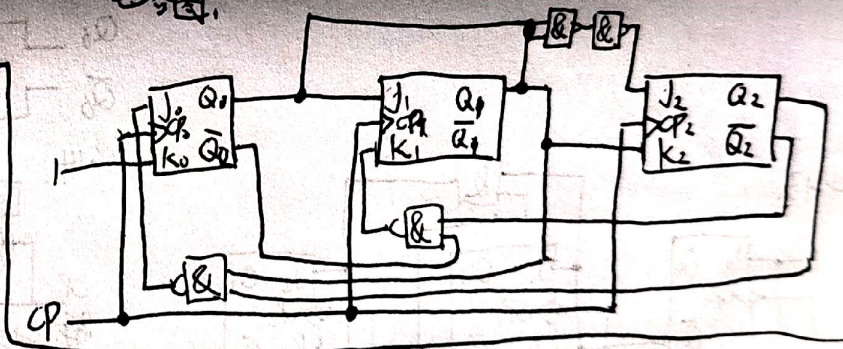

电路图:

